

Uamang 2.0

NCERT

CLASS 10 LIVE

CHAPTER

ELECTRICITY

Electrical
Power &
Energy & it's
Numericals

ABHISHEK SIR



Electric Power & Energy and its numericals

Episode 7

with

ABHISHEK K R

B.Tech - Aerospace, Alliance University

CBSE Expert | Inventor of **RocketPro**

6+ Years Teaching Exp | Mentored **more than 5000 students**

Helped 1000s of students get **10 CGPA** in CBSE X

Vedantu Scholarship Admission Test'20

VSAT 2020

 Grades 6th - 13th

 Every Sunday

REGISTER FOR FREE

vdnt.in/YTVSAT

WHY VSAT?



10+ Crore
worth of
Scholarship pool



**Assured
Scholarships**
upto 100% for
every student giving
the test



FREE Registration
for all students



Online Test
no hassle of going
to a test centre

**THIS EXAM
SEASON**

BOOST YOUR SCORES

LINK - vdnt.in/YTMICRO

ALL MICRO
COURSES
@FLAT

₹ **1**

2000+ Topic wise
Courses

BUY NOW

Class 6-12 | CBSE | ICSE | JEE | NEET



**"I have not failed.
I've just found
10,000 ways that
won't work."**

—THOMAS A. EDISON

ELECTRICITY

Electric Current & Potential Difference

Ohm's Law

Resistance & Factors Affecting it

Resistance in Series

Resistance in Parallel

Heating effects of Electric Current

Electrical Power & Energy

ELECTRICITY

Electric Current & Potential Difference

Ohm's Law

Resistance & Factors Affecting it

Resistance in Series

Resistance in Parallel

Heating effects of Electric Current

Electrical Power & Energy

Umanig 2.0

NCERT

CLASS 10 LIVE

CHAPTER

ELECTRICITY

Heating
Effects of
Electric Current

ABHISHEK SIR





Q1. When a current ' I ' flows through a resistance ' R ' for time ' t ' the electrical energy spent is given by

A

$$IRt$$

B

$$I^2Rt$$

C

$$IR^2t$$

D

$$I^2R/t$$

Q1. When a current ' I ' flows through a resistance ' R ' for time ' t ' the electrical energy spent is given by

A

$$IRt$$

B

$$I^2Rt$$

C

$$IR^2t$$

D

$$I^2R/t$$

Q2. Two electric bulbs have resistances in the ratio 1:2. If they are joined in series, the energy consumed in them is in the ratio.

A

2 : 1

B

1 : 2

C

4 : 1

D

1 : 4

Q2. Two electric bulbs have resistances in the ratio 1:2. If they are joined in series, the energy consumed in them is in the ratio.

Q2. Two electric bulbs have resistances in the ratio 1:2. If they are joined in series, the energy consumed in them is in the ratio.

A

2 : 1

B

1 : 2

C

4 : 1

D

1 : 4

Q3. If the current flowing through a fixed resistor is halved, the heat produced in it will become:

A

One -Fourth

B

One - Half

C

Double

D

Four times

Q3. If the current flowing through a fixed resistor is halved, the heat produced in it will become:

A

One -Fourth

B

One - Half

C

Double

D

Four times

Q9. A current of 5 ampere is passed through a conductor of 12 ohms for 2 minutes. Calculate the amount of heat produced.



ANSWER : 36 KJ

g gangadhar prasad • 1 day ago (edited)
 Answer to h.w question is 36000 Joules. Loved the session a lot!!!! Congratulation Vedantu 9 and 10 for 600k subscribers. Sir plz start a channel for physics too, it will help a lot of students!!!! We will wait for the 600k celebration.

3

A Avyaaz ch • 1 day ago
 Current(I)=5A
 resistance(R)=12ohm
 time(T) =2min=120s
 heat= $I^2 \times R \times T$
 = $25 \times 12 \times 120$

Read more

3

3 replies

Kunal Arya • 1 day ago
 ANSWER-36000 Joules or 36 Kilo Joules...

2





Gamer Piyush • 1 day ago
It's 36k joule



Dablu • 1 day ago (edited)
Homework Q ka Ans is 36000



1



Faizan • 1 day ago
ANSWER IS 36000 J



1



Chaitanya Kashyap • 1 day ago
The correct answer is 36000 J.



3



Tejas Kumar • 1 day ago
36000J is the answer =36Kilo joules



3



Let's take the case of a water heater



Let's take the case of an electric heater

Electric heater converts electric energy to heat energy





Can reach temperatures of 50-60°C

Now consider an electric furnace



Now consider an electric furnace

Electric furnace also converts electrical energy to heat energy





Can reach temperature of around
1000-1200 °C

Which of these devices can consume electric energy turn it to heat energy faster?



Water Heater



Electric Furnace

Which of these devices can consume electric energy turn it to heat energy faster?



Water Heater



Electric Furnace



The **rate of energy consumption** (or heat generation) is more in furnace than water heater.

The **rate of energy consumption** (or heat generation) is more in furnace than water heater.



The **rate of energy consumption** (or heat generation) is more in furnace than water heater.



$$Power = \frac{\text{Energy dissipated}}{\text{time}} = \frac{H}{t} = \frac{V \cdot I \cdot t}{t}$$

$$Power (P) = V \cdot I$$

So which of these device will have more power?



Water Heater



Electric Furnace



Electric Furnace

Electric furnace consumes / dissipates more energy per second

Formulas of Electric power

$$P = V I$$

$$P = V^2 / R$$

$$P = I^2 R$$

$$P = W/t$$

VIP



Vedantu Scholarship Admission Test'20

VSAT 2020

 Grades 6th - 13th

 Every Sunday

REGISTER FOR FREE

vdnt.in/YTVSAT

WHY VSAT?



10+ Crore
worth of
Scholarship pool



**Assured
Scholarships**
upto 100% for
every student giving
the test



FREE Registration
for all students



Online Test
no hassle of going
to a test centre

**THIS EXAM
SEASON**

BOOST YOUR SCORES

LINK - vdnt.in/YTMICRO

ALL MICRO
COURSES
@FLAT

₹ **1**

2000+ Topic wise
Courses

BUY NOW

Class 6-12 | CBSE | ICSE | JEE | NEET

Q4. A bulb of power 100W is connected to a supply of 220V. How much current will it draw from the supply



Q4. A bulb of power 100W is connected to a supply of 220V. How much current will it draw from the supply

1
LEVEL

A

2.2 A

B

0.4545 A

C

0.54 A

D

4.5 A

Q4. A bulb of power 100W is connected to a supply of 220V. How much current will it draw from the supply



Q4. A bulb of power 100W is connected to a supply of 220V. How much current will it draw from the supply

1
LEVEL

A

2.2 A

B

0.4545 A

C

0.54 A

D

4.5 A

Q5. An electric iron has a rating of 750 W, 220 V. Calculate (i) the current flowing through it and (ii) its resistance when in use

[Boards 2011]



Q5. An electric iron has a rating of 750 W, 220 V. Calculate (i) the current flowing through it and (ii) its resistance when in use

[Boards 2011]

2
LEVEL

A

$$I = 2.2 \text{ A}, R = 75.5 \, \Omega$$

B

$$I = 3.4 \text{ A}, R = 75.5 \, \Omega$$

C

$$I = 3.4 \text{ A}, R = 64.53 \, \Omega$$

D

$$I = 0.5 \text{ A}, R = 100 \, \Omega$$

Q5. An electric iron has a rating of 750 W, 220 V. Calculate (i) the current flowing through it and (ii) its resistance when in use

[Boards 2011]



SOLUTION

Given: $P = 750 \text{ W}$, $V = 220 \text{ V}$

(i)

$$P = VI$$

$$750 = 220 \times I$$

\Rightarrow

$$I = \frac{750}{220} = 3.40 \text{ A}$$

(ii)

$$P = \frac{V^2}{R}$$

\Rightarrow

$$R = \frac{V^2}{P} = \frac{220^2}{750} \Rightarrow R = 64.53 \Omega$$

Q5. An electric iron has a rating of 750 W, 220 V. Calculate (i) the current flowing through it and (ii) its resistance when in use

[Boards 2011]

2
LEVEL

A

$$I = 2.2 \text{ A}, R = 75.5 \, \Omega$$

B

$$I = 3.4 \text{ A}, R = 75.5 \, \Omega$$

C

$$I = 3.4 \text{ A}, R = 64.53 \, \Omega$$

D

$$I = 0.5 \text{ A}, R = 100 \, \Omega$$

Q6. The wattage of a bulb is 24 W when it is connected to a 12 V battery. Calculate its effective wattage if it operates on a 6V battery.
[Boards 2011]



Q6. The wattage of a bulb is 24 W when it is connected to a 12 V battery. Calculate its effective wattage if it operates on a 6 V battery.
[Boards 2011]

3
 LEVEL

A

6 W

B

3 W

C

12 W

D

24 W

Q6. The wattage of a bulb is 24 W when it is connected to a 12 V battery. Calculate its effective wattage if it operates on a 6 V battery. (Neglect the change in resistance due to unequal heating of the filament in the two cases.)

[Boards 2011]



SOLUTION

Given: $P_1 = 24 \text{ W}$, $V_1 = 12 \text{ V}$, $P_2 = ?$, $V_2 = 6 \text{ V}$

Using $P = \frac{V^2}{R}$

$$\frac{P_1}{P_2} = \frac{V_1^2}{V_2^2}$$

$$\Rightarrow P_2 = \left(\frac{V_2}{V_1}\right)^2 \times P_1 = \left(\frac{6}{12}\right)^2 \times 24 = \frac{1}{4} \times 24 = 6 \text{ W}$$

Q6. The wattage of a bulb is 24 W when it is connected to a 12 V battery. Calculate its effective wattage if it operates on a 6 V battery.
[Boards 2011]

3
 LEVEL

A

6 W

B

3 W

C

12 W

D

24 W

COMMERCIAL UNIT OF ENERGY

Have you seen a device like this?



Have you seen a device like this?



It measures the **electric energy** that we consume.

There are many **electrical appliances** at home.


And they **consume** a lot of **energy**.

Assume that the power rating of a air conditioner is **500W**



Let us find the energy you use:

.

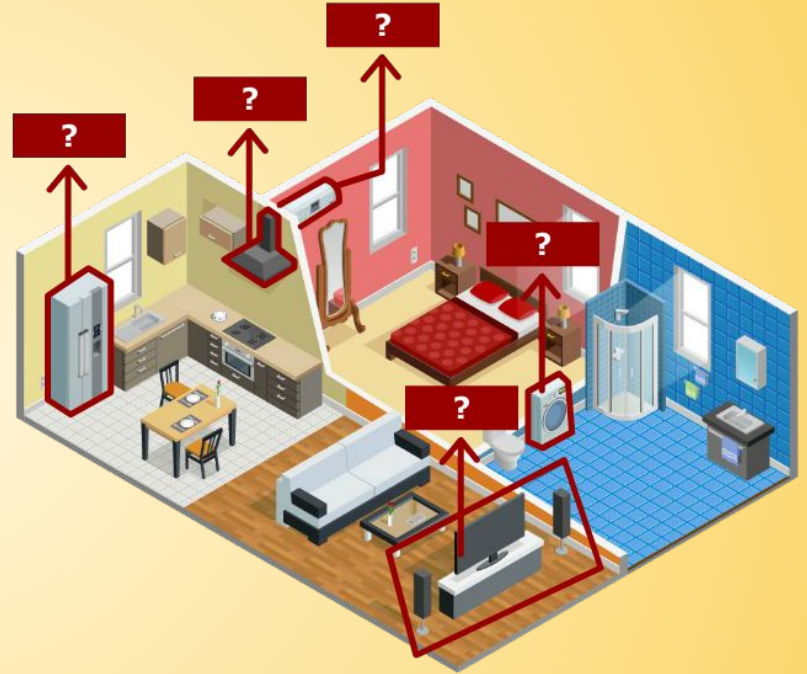

Watts is a very **impractical** unit to measure
home energy consumption

Watts is a very **impractical** unit to measure **home energy consumption**

That is why we use **kWh (KiloWatt - hour)**

Watts is a very **impractical** unit to measure **home energy consumption**

That is why we use **kWh (KiloWatt - hour)**

$$\begin{aligned} 1 \text{ kWh} &= 1000 \times 3600 \text{ W -s} \\ &= 3600000 \text{ J} \\ &= 3.6 \times 10^6 \text{ J} \end{aligned}$$

If you notice carefully, this **device measures** electric energy in **kWh**



This reading helps electric companies **charge** us for **electric energy**.

VIP



Q9. A 100W bulb is operated for 8 hours daily. Find the cost of operating this bulb for 30 days. Assuming the cost of electricity is ₹4 per unit.

1
LEVEL

A

₹ 68

B

₹ 96

C

₹ 112

D

₹ 124

Q9. A 100W bulb is operated for 8 hours daily. Find the cost of operating this bulb for 30 days. Assuming the cost of electricity is ₹4 per unit.



SOLUTION

Given power of the bulb = 100W

Energy consumed by the bulb in a second = 100J

$$\begin{aligned}
 \text{Energy consumed by the bulb in a month} &= 100 \times 3600 \times 8 \times 30 \\
 &= 86400000J \\
 &= \frac{86400000}{3600000} = 24kWh
 \end{aligned}$$

Cost of electric energy = $24 \times 4 = 96$

Q9. A 100W bulb is operated for 8 hours daily. Find the cost of operating this bulb for 30 days. Assuming the cost of electricity is ₹4 per unit.

1
LEVEL

A

₹ 68

B

₹ 96

C

₹ 112

D

₹ 124

Q10. A bulb draws 2A current from a voltage supply of 220V. This bulb is operated for 4 hours in a day. Find the energy consumed by the bulb in 30 days (in kWh)

2
LEVEL

A

52.8

B

61.2

C

78.2

D

45.9

Q10. A bulb draws 2A current from a voltage supply of 220V. This bulb is operated for 4 hours in a day. Find the energy consumed by the bulb in 30 days (in kWh)



SOLUTION

Given

$$I = 2A \quad V = 220V$$

$$P = VI = 220 \times 2 = 440W$$

$$\text{Energy consumed} = 440 \times 3600 \times 4 \times 30 = 190080000J$$

$$\text{Energy consumed} = \frac{190080000}{3600000} = 52.8 \text{ kWh}$$

Q10. A bulb draws 2A current from a voltage supply of 220V. This bulb is operated for 4 hours in a day. Find the energy consumed by the bulb in 30 days (in kWh)

2
LEVEL

A

52.8

B

61.2

C

78.2

D

45.9

Q11. A device consumes 180000000 J of energy in a month. If the cost of electricity per unit is ₹3.5. What is the cost of operating the bulb monthly?

3

LEVEL

A

₹ 125

B

₹ 150

C

₹ 175

D

₹ 200

Q11. A device consumes 180000000 J of energy in a month. If the cost of electricity per unit is ₹3.5. What is the cost of operating the bulb monthly?



SOLUTION

Given

$$\text{Energy consumed} = 180000000J$$

$$\text{Cost} = \frac{3.5}{kWh}$$

$$\text{Cost of operating} = \frac{180000000}{3600000} \times 3.5 = 50 \times 3.5 = 175$$

Q11. A device consumes 180000000 J of energy in a month. If the cost of electricity per unit is ₹3.5. What is the cost of operating the bulb monthly?

3
LEVEL

A

₹ 125

B

₹ 150

C


₹ 175

D

₹ 200

Q12. An electric bulb of resistance 200 ohm draws a current of 1A. Calculate the power of the bulb and energy in KWh consumed burning it for 5 hours.

[Boards 2013]

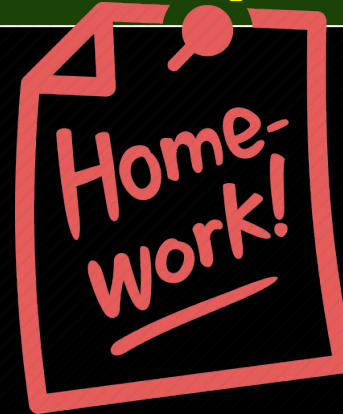

Vedantu Scholarship Admission Test'20

VSAT 2020

 Grades 6th - 13th

 Every Sunday

REGISTER FOR FREE

vdnt.in/YTVSAT

WHY VSAT?



10+ Crore
worth of
Scholarship pool



**Assured
Scholarships**
upto 100% for
every student giving
the test



FREE Registration
for all students



Online Test
no hassle of going
to a test centre

VSAT 2020

Grades 9-10



19950

Students Attended



₹32.31 Cr

Scholarships won



GV Siddarth
Bengaluru

Scholarship Won
100%



Nitish
Jalandhar

Scholarship Won
90%



Himanshu
Hisar

Scholarship Won
90%

**THIS EXAM
SEASON**

BOOST YOUR SCORES

LINK - vdnt.in/YTMICRO

ALL MICRO
COURSES
@FLAT

₹ **1**

2000+ Topic wise
Courses

BUY NOW

Class 6-12 | CBSE | ICSE | JEE | NEET

ELECTRICITY

Electric Current & Potential Difference

Ohm's Law

Resistance & Factors Affecting it

Resistance in Series

Resistance in Parallel

Heating effects of Electric Current

Electrical Power & Energy





Reach out to me @
k.abhishek@vedantu.com